


ECEN 454-508

Lab 3

Nicholas Tann

2/10/2020

## Inverter:

 

## Delays

Rising - 498ps

Falling - 481ps

## Delay Table


Capacitance (f)	Rising Delay (ps)	Falling Delay (ps)	Error %
1	45.2	27.1	66.78
10	101	85.8	17.71
20	144	131	9.92
30	188	175	7.42

40	232	219	5.93
50	277	262	5.72
60	321	306	4.90
70	368	351	4.84
80	410	393	4.32
90	451	439	2.73
100	498	481	3.53


### Capacitance

Frequency (MHz)	Current (uA)	Capacitance (fF)
100	2.06	3.279
200	4.11	3.271
300	6.18	3.279
400	8.24	3.279
500	10.3	3.279
600	12.3	3.263
700	14.4	3.274
800	16.5	3.283
900	18.5	3.272
1000	20.6	3.279

Average Capacitance = 3.2758fF

 

NAND:

 

## Delays

Rising- 701ps  
Falling - 650ps

## Delay Table


Capacitance (f)	Rising Delay (ps)	Falling Delay (ps)	Error %
1	57.7	35.4	62.99
10	125	107	16.82
20	190	168	13.09
30	254	229	10.91
40	320	291	9.96

50	383	351	9.11
60	447	414	7.97
70	511	474	7.80
80	575	533	7.87
90	637	595	7.05
100	701	656	6.85


**Capacitance Table**

Frequency (MHz)	Current (uA)	Capacitance (fF)
100	1.4	2.228
200	2.81	2.2366
300	4.21	2.335
400	5.62	2.36
500	7.02	2.235
600	8.42	2.233
700	9.83	2.235
800	11.2	2.228
900	12.6	2.228
1000	14.0	2.228

Average Capacitance = 2.2322fF

 

XOR:

 

## Delays

Rising - 696ps

Falling - 656ps

## Delay Table

Capacitance (f)	Rising Delay (ps)	Falling Delay (ps)	Error %
1	52.9	39.8	32.91
10	116	103	12.62
20	181	166	9.03
30	247	228	8.33
40	310	290	6.89




50	374	351	6.55
60	439	412	6.55
70	506	474	6.75
80	566	535	5.79
90	633	596	6.20
100	696	656	6.09

### Capacitance

Frequency (MHz)	Current (uA)	Capacitance (fF)
100	4.38	6.971
200	8.74	6.955
300	13.1	6.950
400	17.5	6.963
500	21.8	6.939
600	26.2	6.950
700	30.5	6.935
800	34.9	6.943
900	39.2	6.932
1000	43.6	6.939

Average Capacitance = 6.9477 fF

 

## Cell18.spi

```
//Spice netlist for an inverter simulator lang=spectre subckt IV (input output VDD VSS)
parameters wp=0.6u lp=0.2u wn=0.3u ln=0.3u          M1 output input VDD VDD
tsmc18P w=wp l=lp      M2 output input VSS VSS tsmc18N w=wn l=ln ends IV
```

```
//Spice netlist for NAND subckt NAND (A B output VDD VSS)      parameters wp=0.6u
lp=0.2u wn=0.3u ln=0.2u          M1 output A VDD VDD tsmc18P w=wp l=lp      M2
output B VDD VDD tsmc18P w=wp l=lp      M3 output A w1 VSS tsmc18N w=wn l=ln
M4 w1 B VSS VSS tsmc18N w=wn l=ln ends NAND
```

```
//Spice netlist for an XOR subckt XOR (A B output VDD VSS)  parameters wp=1.2u lp=0.2u
wn=0.3u ln=0.2u
```

```
inv1(A A_not VDD VSS) IV wp=0.9u lp=0.2u wn=0.3u ln=0.2u  inv2(B B_not VDD VSS) IV
wp=0.9u lp=0.2u wn=0.3u ln=0.2u          M1 w1 B VDD VDD tsmc18P w=wp l=lp  M2
output A_not w1 VDD tsmc18P w=wp l=lp  M3 w2 B_not VDD VDD tsmc18P w=wp l=lp  M4
output A w2 VDD tsmc18P w=wp l=lp
```

```
      M5 w3 A_not output VSS tsmc18N w=wn l=ln  M6 VSS B_not w3 VSS tsmc18N w=wn l=ln
M7 w4 A output VSS tsmc18N w=wn l=ln  M8 VSS B w4 VSS tsmc18N w=wn l=ln  ends XOR
```

inverter.spi & inverter\_delaytable.spi

;Spice netlist for an inverter and a capacitor simulator lang=spectre

include "~/ECEN454/Lab1/spectre/model18.spi" include "~/ECEN454/Lab1/spectre/cell18.spi"

vgnd (gnd 0) vsource dc=0 vvdd (vdd 0) vsource dc=1.8

vpwl (IV\_in 0) vsource type=pwl wave=[0n 0 1n 0 1.2n 1.8 4n 1.8 4.2n 0]

X1 (IV\_in IV\_out vdd gnd) IV wp=0.9u lp=0.2u wn=0.3u ln=0.2u

R1 (IV\_out 1) resistor r=1 C1 (1 0) capacitor c=100f

TransientAnalysis tran start=0 stop=10ns step=1ps save IV\_in IV\_out

inverter\_simcap.spi

;Spice netlist for an inverter and a capacitor simulator lang=spectre

include "~/ECEN454/Lab1/spectre/model18.spi" include "~/ECEN454/Lab1/spectre/cell18.spi"

vgnd (gnd 0) vsource dc=0 vvdd (vdd 0) vsource dc=1.8

acinput (IV\_in 0) vsource dc=0 mag=1

R1 (IV\_in IV\_in1) resistor r=0

X1 (IV\_in1 IV\_out vdd gnd) IV wp=0.9u lp=0.2u wn=0.4u ln=0.2u

Freq ac start=1e+1 stop=1e+9 save R1:currents

NAND.spi & NAND\_delaytable.spi

;Spice netlist for NAND and a capacitor simulator lang=spectre

include "~/ECEN454/Lab1/spectre/model18.spi" include "~/ECEN454/Lab1/spectre/cell18.spi"

vgnd (gnd 0) vsource dc=0 vvdd (vdd 0) vsource dc=1.8 vvd (NAND\_B 0) vsource dc=1.8

vpwl (NAND\_A 0) vsource type=pwl wave=[0n 0 1n 0 1.2n 1.8 4n 1.8 4.2n 0]

X1 (NAND\_A NAND\_B NAND\_OUT vdd gnd) NAND wp=0.6u lp=0.2u wn=0.3u ln=0.2u

R1 (NAND\_OUT 1) resistor r=1 C1 (1 0) capacitor c=100f

TransientAnalysis tran start=0 stop=10ns step=1ps save NAND\_A NAND\_B NAND\_OUT

NAND\_simcap.spi

;Spice netlist for an inverter and a capacitor simulator lang=spectre

include "~/ECEN454/Lab1/spectre/model18.spi" include "~/ECEN454/Lab1/spectre/cell18.spi"

vgnd (gnd 0) vsource dc=0 vvdd (vdd 0) vsource dc=1.8 vvd (NAND\_B 0) vsource dc=1.8

acinput (NAND\_A 0) vsource dc=0 mag=1

R1 (NAND\_A NAND\_A1) resistor r=0

X1 (NAND\_A1 NAND\_B NAND\_out vdd gnd) NAND wp=0.6u lp=0.2u wn=0.3u ln=0.2u

Freq ac start=1e+1 stop=1e+9 save R1:currents

XOR.spi & XOR\_delaytable.spi

;Spice netlist for an inverter and a capacitor simulator lang=spectre

include "~/ECEN454/Lab1/spectre/model18.spi" include "~/ECEN454/Lab1/spectre/cell18.spi"

vgnd (gnd 0) vsource dc=0 vvdd (vdd 0) vsource dc=1.8 vvd (XOR\_B 0) vsource dc=1.8

vpwl (XOR\_A 0) vsource type=pwl wave=[0n 0 1n 0 1.2n 1.8 4n 1.8 4.2n 0]

X1 (XOR\_A XOR\_B XOR\_out vdd gnd) XOR wp=1.2u lp=0.2u wn=0.3u ln=0.2u

R1 (XOR\_out 1) resistor r=1 C1 (1 0) capacitor c=100f

TransientAnalysis tran start=0 stop=10ns step=1ps save XOR\_A XOR\_out



XOR\_simcap.spi

;Spice netlist for an inverter and a capacitor simulator lang=spectre

include "~/ECEN454/Lab1/spectre/model18.spi" include "~/ECEN454/Lab1/spectre/cell18.spi"

vgnd (gnd 0) vsource dc=0 vvdd (vdd 0) vsource dc=1.8 vvd (XOR\_B 0) vsource dc=1.8

acinput (XOR\_A 0) vsource dc=0 mag=1

R1 (XOR\_A XOR\_A1) resistor r=0

X1 (XOR\_A1 XOR\_B XOR\_out vdd gnd) XOR wp=1.2u lp=0.2u wn=0.3u ln=0.2u

Freq ac start=1e+1 stop=1e+9 save R1:currents