

Nicholas Tann


HW 1

ECEN 449-503

2/9/2020

Problem #1:

Waveform

 

Structural Verilog

```
module QOneStructural (input A, input B, input C, input D,
```

```
output E, output F
```

```
);
```

```
wire X, Y, Z;
```

```
//explicitly creating the gates by initiating them as their names from the diagram, io corresponds  
to io from diagram
```

```
not not2 (X, A);
```

```
    and and2 (Y, A, B);

    or or2 (Z, Y, C);

    or or1 (E, X, Z);

    nand nand2 (F, Z, D);

endmodule
```

Data Flow Verilog

```
module QOneDataflow (input A, input B, input C, input D,

                    output E, output F                );

    wire X, Y, Z;

    assign X = ~A; //output of NOT2

    assign Y = A & B; //output of AND2

    assign Z = Y | C; //output of OR2

    assign E = X | Z; //output of OR1
```

```
assign F = Z ~& D; //output NAND2
```

```
endmodule
```

Behavioral Verilog

```
module QOneBehavioral (input A, input B, input C, input D,
```

```
output E, output F      );
```

```
reg E, F;
```

```
always @(A or B or C or D)
```

```
    //boolean algebra output for E given A,B,C,D
```

```
    if (A == 0) E = 1;
```

```
    else if (C == 1) E = 1;
```

```
    else if (B == 1) E = 1;
```

```
    else E = 0;
```

//boolean algebra output for F given A,B,C,D

if (D == 0) F = 1;

else if (A == 0) begin

if (C == 0) F = 1;

else F = 0;

end

else if (B == 0) begin

if (C == 0) F = 1;

else F = 0;

end

else F = 0;

end

endmodule

FSM

